

Questions

- What is a truth table?
- Write the truth tables for AND, OR, NOT, NOR, NAND, XOR
- What is DeMorgans Theorem?
- What is a logic unit?
- How does a selector work?
- How does a decoder work?
- What is a multiplexer?
- How does a half adder work?
- How does a full adder work?
- How do we get the full adder to perform subtraction?